
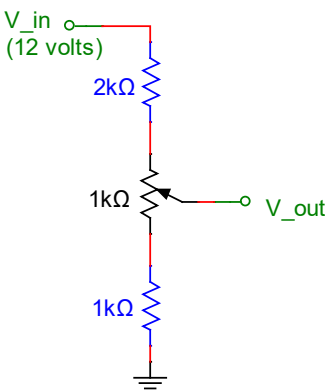


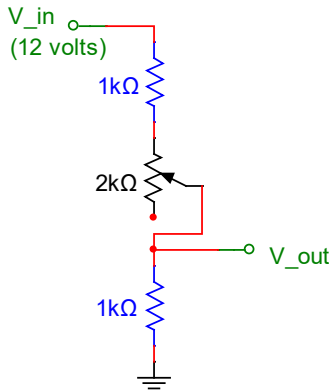


Design #1:

Right way to make
a voltage divider.



Design #2:

Needlessly janky.
Don't do this.

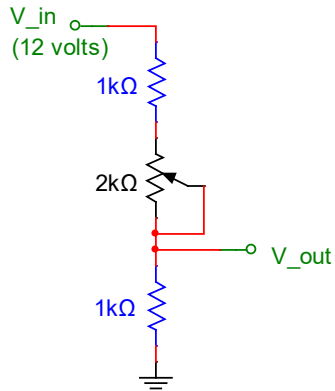

Design #3:

Slightly less janky, but
don't do this either.